



Whack-a-Mole Game on Basys 3 FPGA

TEAM: LogicForge

MEMBERS:

S Ujwal Niranjana

Sucheth Agar R

Kushal S



Contents

1	Project Overview	2
1.1	Objective	2
1.2	Scope	2
1.3	Applications	2
2	System Architecture	3
2.1	Block Diagram	3
2.2	Components	4
3	Modules and Implementation	5
3.1	Clock Division	5
3.2	Counters	7
3.3	Game Logic	8
3.4	Binary to BCD Conversion	23
3.5	Multiplexer and Decoder	27
3.6	Seven-Segment Display	28
3.7	Top module	29
3.8	Constraints	30
4	Testing and Results	33
4.1	Simulation Results	33
4.2	Hardware Testing	33
5	Conclusion and Future Work	34
5.1	Conclusion	34
5.2	Future Enhancements	34



Chapter 1

Project Overview

1.1 Objective

To design and implement a **Whack-a-Mole** game on the Basys 3 FPGA board, utilizing its hardware resources such as LEDs, seven-segment displays, and a clock module. The game includes score tracking and a countdown timer.

1.2 Scope

This project demonstrates the use of FPGA hardware for creating interactive games. It combines multiple hardware modules, including clock dividers, counters, multiplexers, and decoders, to achieve a functional game system.

1.3 Applications

- Educational tools for learning FPGA programming and digital design.
- Interactive gaming applications.
- Demonstration of hardware-based real-time systems.

Chapter 2

System Architecture

2.1 Block Diagram

The system is designed as shown in the block diagram below:

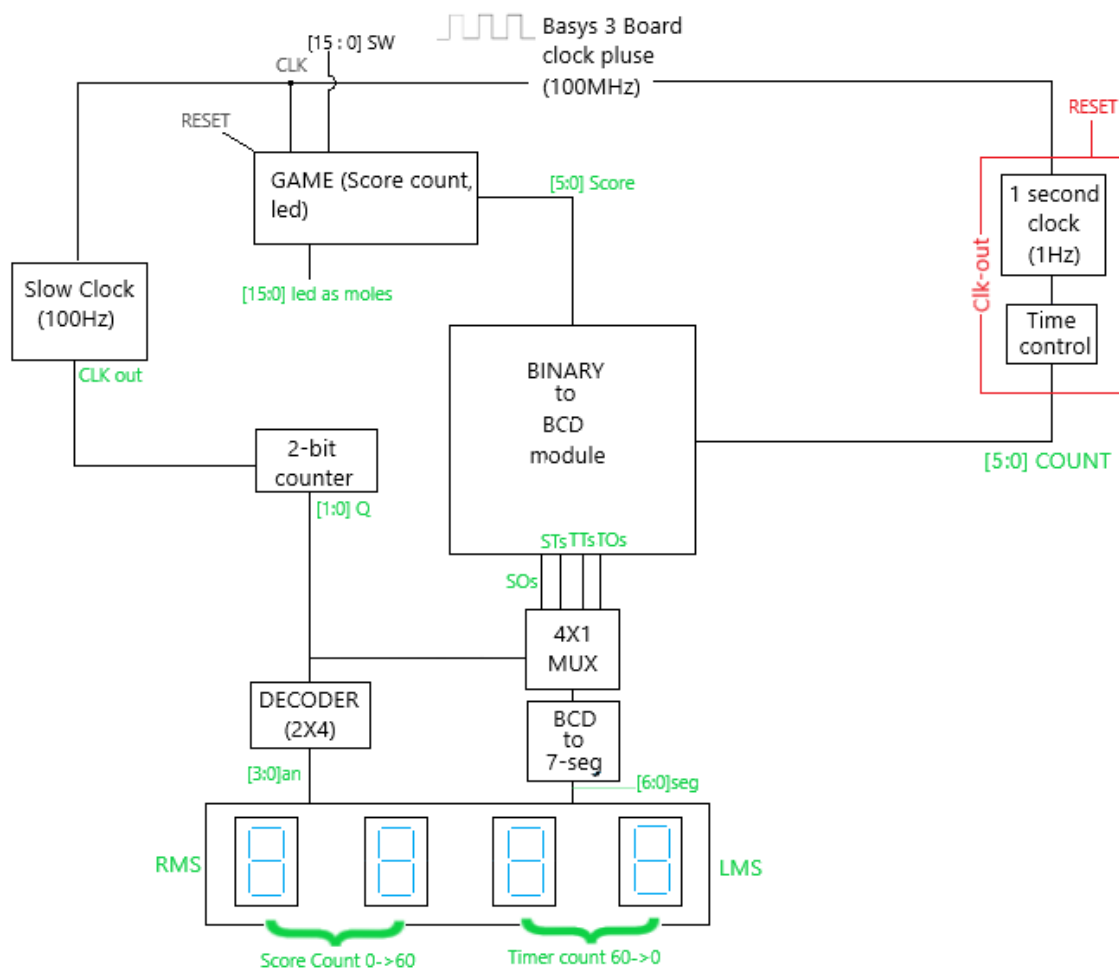


Figure 2.1: Block Diagram of Whack-a-Mole on Basys 3



2.2 Components

1. Clock Modules:

- A 1 Hz clock derived from the 100 MHz board clock to control the countdown timer.
- A slower clock for controlling LED transitions.

2. Game Module:

- Tracks the user's score based on switch inputs.
- Uses a 5-bit score counter to update the score.

3. Binary to BCD Converter:

- Converts binary values of the timer and score into BCD format for display.

4. Multiplexer and Decoder:

- The multiplexer selects between timer and score outputs for display.
- A 2-to-4 decoder drives the seven-segment displays.

5. Seven-Segment Displays:

- Four displays show the countdown timer and score in real-time.

6. LEDs and Switches:

- LEDs simulate the “moles” in the game.
- Switches serve as inputs for “hitting” the mole.



Chapter 3

Modules and Implementation

3.1 Clock Division

Objective: Generate slower clocks from the 100 MHz onboard clock.

Implementation: A clock divider module is designed to generate a 1 Hz clock for the countdown timer and a slower clock for LED transitions.

Listing 3.1: 0.01 seconds clock

```
module slowclk(  
    input clk,  
    output reg clk_out  
);  
    reg [18:0] counter;  
    always @(posedge clk)  
    begin  
        counter <= counter + 1;  
        if(counter == 500_000)  
        begin  
            counter <= 0;  
            clk_out = ~clk_out;  
        end  
    end  
endmodule
```

Listing 3.2: 1 second clock

```
module sec_clk(  
    input clk,  
    output reg clk_o  
);  
    reg [25:0] counter;  
    always @(posedge clk)  
    begin  
        counter <= counter + 1;  
        if(counter == 50_000_000)  
        begin  
            counter <= 0;  
        end  
    end  
endmodule
```



```
        clk_o = ~clk_o;  
    end  
end  
endmodule
```



3.2 Counters

Objective: There are 2 counters. 1st for the timer and the 2nd for the 2-bit counter.

Implementation: 1st counter counts from 60 to 0. 2nd counter controls the mux selectline and also the input to the decoder.

Listing 3.3: Timer counter(downcounter)

```
module timer(  
    input clk_o ,  
    input rst ,  
    output reg [5:0] count  
);  
    always @(clk_o)  
    begin  
        count = 6'b111100;  
        if(rst == 1)  
            count <= 6'b111100;  
        else  
            count <= count - 1;  
        end  
    endmodule
```

Listing 3.4: 2-bit counter(upcounter)

```
module counter(  
    input clk_out ,  
    output reg [1:0]Q  
);  
    always @(posedge clk_out)  
    begin  
        if(Q == 3)  
            Q = 0;  
        else  
            Q = Q + 1;  
        end  
    endmodule
```




3.3 Game Logic

Objective: Track the score based on user inputs.

Implementation: A 5-bit counter increments the score when the correct switch is pressed. The module also interfaces with the LED controller to simulate mole behavior.

Listing 3.5: Game

```
module game(  
    input  [15:0] sw,  
    input  clk , rst ,  
    output reg [15:0] led ,  
    output reg [5:0] score  
);  
  
localparam  
S000000 = 0 ,  
S000001 = 1 ,  
S000010 = 2 ,  
S000011 = 3 ,  
S000100 = 4 ,  
S000101 = 5 ,  
S000110 = 6 ,  
S000111 = 7 ,  
S001000 = 8 ,  
S001001 = 9 ,  
S001010 = 10 ,  
S001011 = 11 ,  
S001100 = 12 ,  
S001101 = 13 ,  
S001110 = 14 ,  
S001111 = 15 ,  
S010000 = 16 ,  
S010001 = 17 ,  
S010010 = 18 ,  
S010011 = 19 ,  
S010100 = 20 ,  
S010101 = 21 ,  
S010110 = 22 ,  
S010111 = 23 ,  
S011000 = 24 ,  
S011001 = 25 ,  
S011010 = 26 ,  
S011011 = 27 ,  
S011100 = 28 ,  
S011101 = 29 ,  
S011110 = 30 ,  
S011111 = 31 ,  
S100000 = 32 ,  
S100001 = 33 ,
```



```
S100010 = 34,  
S100011 = 35,  
S100100 = 36,  
S100101 = 37,  
S100110 = 38,  
S100111 = 39,  
S101000 = 40,  
S101001 = 41,  
S101010 = 42,  
S101011 = 43,  
S101100 = 44,  
S101101 = 45,  
S101110 = 46,  
S101111 = 47,  
S110000 = 48,  
S110001 = 49,  
S110010 = 50,  
S110011 = 51,  
S110100 = 52,  
S110101 = 53,  
S110110 = 54,  
S110111 = 55,  
S111000 = 56,  
S111001 = 57,  
S111010 = 58,  
S111011 = 59,  
S111100 = 60;
```

```
    reg [6:0] current_state = 0;  
    reg [6:0] next_state = 0;  
  
    always @(posedge clk)  
    begin  
        if(rst)  
            current_state <= S000000;  
        else  
            current_state <= next_state;  
        end  
  
    always @(current_state , sw[15:0])  
    begin  
        case(current_state)  
        S000000:  
            begin  
                next_state <= S000000;  
                led[15:0] = 0;  
                score = 6'b000000;  
            end  
        endcase  
    end
```



```
    led[3] <= 1;
    if(sw[3])
        next_state <= S000001;
    else
        next_state <= S000000;
    end
S000001:
    begin
        score <= 6'b000001;
        led[15:0] = 0;
        led[12] <= 1;
        if(sw[12])
            next_state <= S000100;
        else
            next_state <= S000001;
        end
S000010:
    begin
        score <= 6'b000010;
        led[15:0] = 0;
        led[7] <= 1;
        if(sw[7])
            next_state <= S000011;
        else
            next_state <= S000010;
        end
S000011:
    begin
        score <= 6'b000011;
        led[15:0] = 0;
        led[5] <= 1;
        if(sw[5])
            next_state <= S000100;
        else
            next_state <= S000011;
        end
S000100:
    begin
        score <= 6'b000100;
        led[15:0] = 0;
        led[1] <= 1;
        if(sw[1])
            next_state <= S000101;
        else
            next_state <= S000100;
        end
S000101:
    begin
```



```
score <= 6'b0000101;
led[15:0] = 0;
led[11] <= 1;
if(sw[11])
    next_state = S000110;
else
    next_state <= S000101;
end
S000110:
begin
score <= 6'b000110;
led[15:0] = 0;
led[15] <= 1;
if(sw[15])
    next_state <= S000111;
else
    next_state <= S000110;
end
S000111:
begin
score <= 6'b000111;
led[15:0] = 0;
led[14] <= 1;
if(sw[14])
    next_state <= S001000;
else
    next_state <= S000111;
end
S001000:
begin
score <= 6'b001000;
led[15:0] = 0;
led[6] <= 1;
if(sw[6])
    next_state <= S001001;
else
    next_state <= S001000;
end
S001001:
begin
score <= 6'b001001;
led[15:0] = 0;
led[9] <= 1;
if(sw[9])
    next_state <= S001010;
else
    next_state <= S001001;
end
```



```
S001010:
    begin
        score <= 6'b001010;
        led[15:0] = 0;
        led[4] <= 1;
        if(sw[4])
            next_state <= S001011;
        else
            next_state <= S001010;
        end
S001011:
    begin
        score <= 6'b001011;
        led[15:0] = 0;
        led[8] <= 1;
        if(sw[8])
            next_state <= S001100;
        else
            next_state <= S001011;
        end
S001100:
    begin
        score <= 6'b001100;
        led[15:0] = 0;
        led[13] <= 1;
        if(sw[13])
            next_state <= S001101;
        else
            next_state <= S001100;
        end
S001101:
    begin
        score <= 6'b001101;
        led[15:0] = 0;
        led[10] <= 1;
        if(sw[10])
            next_state <= S001110;
        else
            next_state <= S001101;
        end
S001110:
    begin
        score <= 6'b001110;
        led[15:0] = 0;
        led[2] <= 1;
        if(sw[2])
            next_state <= S001111;
        else
```



```
        next_state <= S001110;
    end
S001111:
    begin
        score <= 6'b001111;
        led[15:0] = 0;
        led[1] <= 1;
        if(sw[1])
            next_state <= S010000;
        else
            next_state <= S001111;
        end
S010000:
    begin
        score <= 6'b010000;
        led[15:0] = 0;
        led[6] <= 1;
        if(sw[6])
            next_state <= S010001;
        else
            next_state <= S010000;
        end
S010001://this is where you should stare
    begin
        score <= 6'b010001;
        led[15:0] = 0;
        led[5] <= 1;
        if(sw[5])
            next_state <= S010010;
        else
            next_state <= S010001;
        end
S010010:
    begin
        score <= 6'b010010;
        led[15:0] = 0;
        led[8] <= 1;
        if(sw[8])
            next_state <= S010011;
        else
            next_state <= S010010;
        end
S010011:
    begin
        score <= 6'b010011;
        led[15:0] = 0;
        led[9] <= 1;
        if(sw[9])
```



```
        next_state <= S010100;
    else
        next_state <= S010011;
    end
S010100:
    begin
        score <= 6'b010100;
        led[15:0] = 0;
        led[7] <= 1;
        if(sw[7])
            next_state <= S010101;
        else
            next_state <= S010100;
        end
S010101:
    begin
        score <= 6'b010101;
        led[15:0] = 0;
        led[11] <= 1;
        if(sw[11])
            next_state <= S010110;
        else
            next_state <= S010101;
        end
S010110:
    begin
        score <= 6'b010110;
        led[15:0] = 0;
        led[3] <= 1;
        if(sw[3])
            next_state <= S010111;
        else
            next_state <= S010110;
        end
S010111:
    begin
        score <= 6'b010111;
        led[15:0] = 0;
        led[15] <= 1;
        if(sw[15])
            next_state <= S011000;
        else
            next_state <= S010111;
        end
S011000:
    begin
        score <= 6'b011000;
        led[15:0] = 0;
```



```
    led[13] <= 1;
    if(sw[13])
        next_state <= S011001;
    else
        next_state <= S011000;
    end
S011001:
    begin
        score <= 6'b011001;
        led[15:0] = 0;
        led[4] <= 1;
        if(sw[4])
            next_state <= S011010;
        else
            next_state <= S011001;
        end
S011010:
    begin
        score <= 6'b011010;
        led[15:0] = 0;
        led[12] <= 1;
        if(sw[12])
            next_state <= S011011;
        else
            next_state <= S011010;
        end
S011011:
    begin
        score <= 6'b011011;
        led[15:0] = 0;
        led[2] <= 1;
        if(sw[2])
            next_state <= S011100;
        else
            next_state <= S011011;
        end
S011100:
    begin
        score <= 6'b011100;
        led[15:0] = 0;
        led[10] <= 1;
        if(sw[10])
            next_state <= S011101;
        else
            next_state <= S011100;
        end
S011101:
    begin
```




```
score <= 6'b011101;
led[15:0] = 0;
led[14] <= 1;
if(sw[14])
    next_state <= S011110;
else
    next_state <= S011101;
end
S011110:
begin
score <= 6'b011110;
led[15:0] = 0;
led[1] <= 1;
if(sw[1])
    next_state <= S011111;
else
    next_state <= S011110;
end
S011111:
begin
score <= 6'b011111;
led[15:0] = 0;
led[5] <= 1;
if(sw[5])
    next_state <= S100000;
else
    next_state <= S011111;
end
S100000:
begin
score <= 6'b100000;
led[15:0] = 0;
led[3] <= 1;
if(sw[3])
    next_state <= S100001;
else
    next_state <= S100000;
end
S100001:
begin
score <= 6'b100001;
led[15:0] = 0;
led[8] <= 1;
if(sw[8])
    next_state <= S100010;
else
    next_state <= S100001;
end
end
```



```
S100010:
    begin
        score <= 6'b100010;
        led[15:0] = 0;
        led[6] <= 1;
        if(sw[6])
            next_state <= S100011;
        else
            next_state <= S100010;
        end
S100011:
    begin
        score <= 6'b100011;
        led[15:0] = 0;
        led[2] <= 1;
        if(sw[2])
            next_state <= S100100;
        else
            next_state <= S100011;
        end
S100100:
    begin
        score <= 6'b100100;
        led[15:0] = 0;
        led[12] <= 1;
        if(sw[12])
            next_state <= S100101;
        else
            next_state <= S100100;
        end
S100101:
    begin
        score <= 6'b100101;
        led[15:0] = 0;
        led[15] <= 1;
        if(sw[15])
            next_state <= S100110;
        else
            next_state <= S100101;
        end
S100110:
    begin
        score <= 6'b100110;
        led[15:0] = 0;
        led[9] <= 1;
        if(sw[9])
            next_state <= S100111;
        else
```



```
        next_state <= S100110;
    end
S100111:
    begin
        score <= 6'b010110;
        led[15:0] = 0;
        led[7] <= 1;
        if(sw[7])
            next_state <= S101000;
        else
            next_state <= S100111;
        end
    end
S101000:
    begin
        score <= 6'b101000;
        led[15:0] = 0;
        led[4] <= 1;
        if(sw[4])
            next_state <= S101001;
        else
            next_state <= S101000;
        end
    end
S101001:
    begin
        score <= 6'b101001;
        led[15:0] = 0;
        led[10] <= 1;
        if(sw[10])
            next_state <= S101010;
        else
            next_state <= S101001;
        end
    end
S101010:
    begin
        score <= 6'b101010;
        led[15:0] = 0;
        led[13] <= 1;
        if(sw[13])
            next_state <= S101011;
        else
            next_state <= S101010;
        end
    end
S101011:
    begin
        score <= 6'b101011;
        led[15:0] = 0;
        led[11] <= 1;
        if(sw[11])
```



```
        next_state <= S101100;
    else
        next_state <= S101011;
    end
S101100:
    begin
        score <= 6'b101100;
        led[15:0] = 0;
        led[14] <= 1;
        if(sw[14])
            next_state <= S101101;
        else
            next_state <= S101100;
        end
S101101:
    begin
        score <= 6'b101101;
        led[15:0] = 0;
        led[6] <= 1;
        if(sw[6])
            next_state <= S101110;
        else
            next_state <= S101101;
        end
S101110:
    begin
        score <= 6'b101110;
        led[15:0] = 0;
        led[9] <= 1;
        if(sw[9])
            next_state <= S101111;
        else
            next_state <= S101110;
        end
S101111:
    begin
        score <= 6'b101111;
        led[15:0] = 0;
        led[2] <= 1;
        if(sw[2])
            next_state <= S110000;
        else
            next_state <= S101111;
        end
S110000:
    begin
        score <= 6'b110000;
        led[15:0] = 0;
```



```
    led[8] <= 1;
    if(sw[8])
        next_state <= S110001;
    else
        next_state <= S110000;
    end
S110001:
    begin
        score <= 6'b110001;
        led[15:0] = 0;
        led[13] <= 1;
        if(sw[13])
            next_state <= S110010;
        else
            next_state <= S110001;
        end
S110010:
    begin
        score <= 6'b110010;
        led[15:0] = 0;
        led[15] <= 1;
        if(sw[15])
            next_state <= S110011;
        else
            next_state <= S110010;
        end
S110011:
    begin
        score <= 6'b110011;
        led[15:0] = 0;
        led[3] <= 1;
        if(sw[3])
            next_state <= S110100;
        else
            next_state <= S110011;
        end
S110100:
    begin
        score <= 6'b110100;
        led[15:0] = 0;
        led[12] <= 1;
        if(sw[12])
            next_state <= S110101;
        else
            next_state <= S110100;
        end
S110101:
    begin
```



```
score <= 6'b110101;
led[15:0] = 0;
led[1] <= 1;
if(sw[1])
    next_state <= S110110;
else
    next_state <= S110101;
end
S110110:
begin
score <= 6'b110110;
led[15:0] = 0;
led[5] <= 1;
if(sw[5])
    next_state <= S110111;
else
    next_state <= S110110;
end
S110111:
begin
score <= 6'b110111;
led[15:0] = 0;
led[7] <= 1;
if(sw[7])
    next_state <= S111000;
else
    next_state <= S110111;
end
S111000:
begin
score <= 6'b111000;
led[15:0] = 0;
led[10] <= 1;
if(sw[10])
    next_state <= S111001;
else
    next_state <= S111000;
end
S111001:
begin
score <= 6'b111001;
led[15:0] = 0;
led[4] <= 1;
if(sw[4])
    next_state <= S111010;
else
    next_state <= S111001;
end
```



```
S111010:
    begin
        score <= 6'b111010;
        led[15:0] = 0;
        led[14] <= 1;
        if(sw[14])
            next_state <= S111011;
        else
            next_state <= S111010;
        end
S111011:
    begin
        score <= 6'b111011;
        led[15:0] = 0;
        led[11] <= 1;
        if(sw[11])
            next_state <= S111100;
        else
            next_state <= S111011;
        end
S111100:
    begin
        next_state <= S111100;
        score <= 6'b111100;
        led[15:0] <= 0;
    end
endcase
end
endmodule
```



3.4 Binary to BCD Conversion

Objective: Convert binary values of score and timer into BCD format.

Implementation: A binary to BCD conversion module is implemented to ensure compatibility with the seven-segment displays.

- Shift the binary number left one bit.
- If 8 shifts have taken place, the BCD number is in the Hundreds, Tens, and Units column.
- If the binary value in any of the BCD columns is 5 or greater, add 3 to that value in that BCD column.
- Go to 1.


Operation	Tens	Units	Binary
HEX			E
Start			1 1 1 0
Shift 1		1	1 1 0
Shift 2		1 1	1 0
Shift 3		1 1 1	0
Add 3		1 0 1 0	0
Shift 4	1	0 1 0 0	
BCD	1	4	

Figure 3.1: Convert hex E to BCD

Operation	Hundreds	Tens	Units	Binary	
HEX				F	F
Start				1 1 1 1	1 1 1 1
Shift 1			1	1 1 1 1	1 1 1
Shift 2			1 1	1 1 1 1	1 1
Shift 3			1 1 1	1 1 1 1	1
Add 3			1 0 1 0	1 1 1 1	1
Shift 4		1	0 1 0 1	1 1 1 1	
Add 3		1	1 0 0 0	1 1 1 1	
Shift 5		1 1	0 0 0 1	1 1 1	
Shift 6		1 1 0	0 0 1 1	1 1	
Add 3		1 0 0 1	0 0 1 1	1 1	
Shift 7	1	0 0 1 0	0 1 1 1	1	
Add 3	1	0 0 1 0	1 0 1 0	1	
Shift 8	1 0	0 1 0 1	0 1 0 1		
BCD	2	5	5		

Figure 3.2: Convert hex FF to BCD

A3 A2 A1 A0

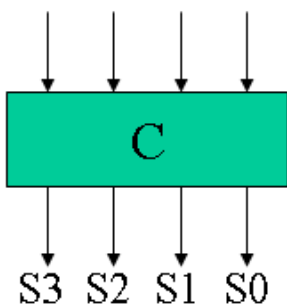

S3 S2 S1 S0

A3	A2	A1	A0	S3	S2	S1	S0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	1
0	1	0	0	0	1	0	0
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Figure 3.3: Truth table for Add-3 Module

Listing 3.6: Shift add 3 algorithm

```

module shift_add3(
    input [3:0] in ,
    output reg [3:0] out
);
always @(in)
begin
    case(in)
        4'b0000 : out <= 4'b0000;
        4'b0001 : out <= 4'b0001;
        4'b0010 : out <= 4'b0010;
        4'b0011 : out <= 4'b0011;
        4'b0100 : out <= 4'b0100;
        4'b0101 : out <= 4'b1000;
        4'b0110 : out <= 4'b1001;
        4'b0111 : out <= 4'b1010;
        4'b1000 : out <= 4'b1011;
        4'b1001 : out <= 4'b1100;
    endcase
end
endmodule

```

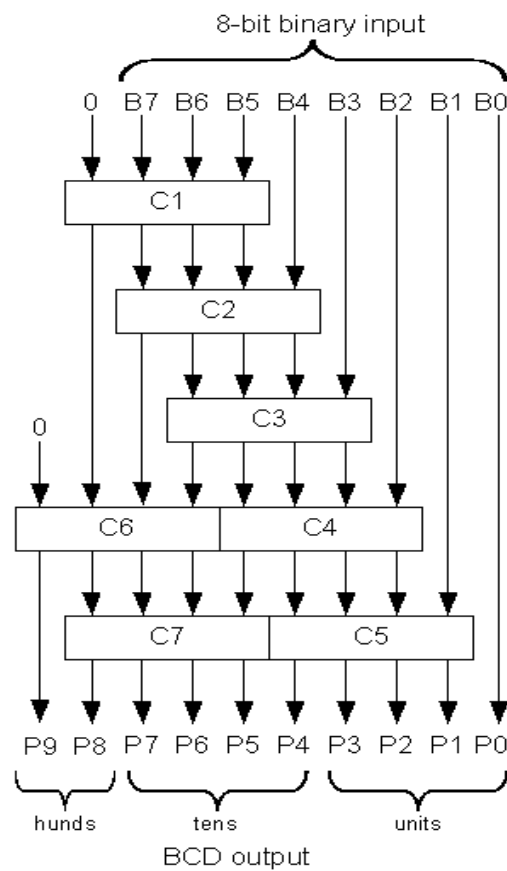


Figure 3.4: Binary-to-BCD Converter Module



Listing 3.7: Binary to BCD

```
module Bin_to_Bcd(  
    input [5:0] inp ,  
    output [3:0] ones ,  
    output [3:0] tens  
);  
    wire [3:0] c1 , c2 , c3 , c4 , c5 , c6 , c7 ;  
    wire [3:4] d1 , d2 , d3 , d4 , d5 , d6 , d7 ;  
  
    assign d1 = {3'b000 , inp [5]} ;  
    assign d2 = {c1 [2:0] , inp [4]} ;  
    assign d3 = {c2 [2:0] , inp [3]} ;  
    assign d4 = {c3 [2:0] , inp [2]} ;  
    assign d5 = {c4 [2:0] , inp [1]} ;  
    assign d6 = {1'b0 , c1 [3] , c2 [3] , c3 [3]} ;  
    assign d7 = {c6 [2:0] , c4 [3]} ;  
  
    shift_add3 SA1(.in(d1) , .out(c1)) ;  
    shift_add3 SA2(.in(d2) , .out(c2)) ;  
    shift_add3 SA3(.in(d3) , .out(c3)) ;  
    shift_add3 SA4(.in(d4) , .out(c4)) ;  
    shift_add3 SA5(.in(d5) , .out(c5)) ;  
    shift_add3 SA6(.in(d6) , .out(c6)) ;  
    shift_add3 SA7(.in(d7) , .out(c7)) ;  
  
    assign ones = {c5 [2:0] , inp [0]} ;  
    assign tens = {c7 [2:0] , c5 [3]} ;  
endmodule
```



3.5 Multiplexer and Decoder

Objective: Manage the display of timer and score on the seven-segment displays.

Implementation:

- A 4-to-1 multiplexer selects between timer and score outputs.
- A 2-to-4 decoder drives the seven-segment displays.

Listing 3.8: Decoder

```
module decoder(  
    input  [1:0] Q,  
    output reg [3:0] an  
);  
    always @(Q)  
    begin  
        case(Q)  
            2'b00: an <= 4'b0001;  
            2'b01: an <= 4'b0010;  
            2'b10: an <= 4'b0100;  
            2'b11: an <= 4'b1000;  
        endcase  
    end  
endmodule
```

Listing 3.9: Multiplexer

```
module mux(  
    input  [3:0] To,Tt,So,St ,  
    input  [1:0] Q,  
    output reg [3:0] Y  
);  
    always @(To or Tt or So or St or Q)  
    begin  
        case(Q)  
            2'b00 : Y = Tt;  
            2'b01 : Y = To;  
            2'b10 : Y = St;  
            2'b11 : Y = So;  
        endcase  
    end  
endmodule
```



3.6 Seven-Segment Display

Objective: Display the countdown timer and score.

Implementation: A BCD-to-seven-segment decoder drives the displays. Each segment is updated in real-time based on the game logic.

Listing 3.10: BCD to seven segment

```
module bcd_to_7seg(  
    input [3:0] Y,  
    output reg [6:0] seg  
);  
    always @(Y)  
    begin  
        case(Y)  
            4'b0000 : seg <= 7'b0000001;  
            4'b0001 : seg <= 7'b1001111;  
            4'b0010 : seg <= 7'b0010010;  
            4'b0011 : seg <= 7'b0000110;  
            4'b0100 : seg <= 7'b1001100;  
            4'b0101 : seg <= 7'b0100100;  
            4'b0110 : seg <= 7'b0100000;  
            4'b0111 : seg <= 7'b0001111;  
            4'b1000 : seg <= 7'b0000000;  
            4'b1001 : seg <= 7'b0001100;  
        endcase  
    end  
endmodule
```



3.7 Top module

Objective: Integrate all the modules.

Implementation: All the modules are initialized in this module and the input and output of the system is declared.

Listing 3.11: Top Module

```
module top_module(  
    input  clk , rst ,  
    input  [15:0] sw ,  
    output [15:0] led ,  
    output [6:0] seg ,  
    output [3:0] an  
);  
  
    wire clk_out ;  
    wire timer_clk_out ;  
    wire [3:0] mux_out ;  
    wire [1:0] counter_out ;  
    wire [3:0] To,Tt,So,St ;  
    wire [5:0] score ;  
    wire [5:0] timer ;  
  
    Bin_to_Bcd UBCD1(.inp(score) ,.ones(So) ,.tens(St));  
    Bin_to_Bcd UBCD2(.inp(timer) ,.ones(To) ,.tens(Tt));  
  
    mux UMUX(.To(To) ,.Tt(Tt) ,.So(So) ,.St(St) ,.Q(counter_out) ,.Y(mux_out));  
  
    slowclk USCK(.clk(clk) ,.clk_out(clk_out));  
  
    counter U2BC(.clk_out(clk_out) ,.Q(counter_out));  
  
    decoder UD(.Q(counter_out) ,.an(an));  
  
    bcd_to_7seg UBCDSEG(.Y(mux_out) ,.seg(seg));  
  
    sec_clk USC(.clk(clk) ,.clk_o(timer_clk_out));  
  
    timer UT(.clk_o(timer_clk_out) ,.rst(rst) ,.count(timer));  
  
    game UG(.sw(sw) ,.clk(clk) ,.led(led) ,.rst(rst) ,.score(score));  
  
endmodule
```



3.8 Constraints

Objective: Show where the inputs and outputs of the module is present on the basys 3 board.

Implementation: All the ports are mapped on the basys 3 Board.

Listing 3.12: Constraints

```
# Clock signal
set_property PACKAGEPIN W5 [get_ports clk]
    set_property IOSTANDARD LVCMOS33 [get_ports clk]
    create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5}

# Switches
set_property PACKAGEPIN V17 [get_ports {sw[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[0]}]
set_property PACKAGEPIN V16 [get_ports {sw[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[1]}]
set_property PACKAGEPIN W16 [get_ports {sw[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[2]}]
set_property PACKAGEPIN W17 [get_ports {sw[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[3]}]
set_property PACKAGEPIN W15 [get_ports {sw[4]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[4]}]
set_property PACKAGEPIN V15 [get_ports {sw[5]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[5]}]
set_property PACKAGEPIN W14 [get_ports {sw[6]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[6]}]
set_property PACKAGEPIN W13 [get_ports {sw[7]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[7]}]
set_property PACKAGEPIN V2 [get_ports {sw[8]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[8]}]
set_property PACKAGEPIN T3 [get_ports {sw[9]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[9]}]
set_property PACKAGEPIN T2 [get_ports {sw[10]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[10]}]
set_property PACKAGEPIN R3 [get_ports {sw[11]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[11]}]
set_property PACKAGEPIN W2 [get_ports {sw[12]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[12]}]
set_property PACKAGEPIN U1 [get_ports {sw[13]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[13]}]
set_property PACKAGEPIN T1 [get_ports {sw[14]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[14]}]
set_property PACKAGEPIN R2 [get_ports {sw[15]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sw[15]}]

# LEDs
set_property PACKAGEPIN U16 [get_ports {led[0]}]
```



```
        set_property IOSTANDARD LVCMOS33 [get_ports {led[0]}]
set_property PACKAGEPIN E19 [get_ports {led[1]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[1]}]
set_property PACKAGEPIN U19 [get_ports {led[2]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[2]}]
set_property PACKAGEPIN V19 [get_ports {led[3]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[3]}]
set_property PACKAGEPIN W18 [get_ports {led[4]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[4]}]
set_property PACKAGEPIN U15 [get_ports {led[5]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[5]}]
set_property PACKAGEPIN U14 [get_ports {led[6]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[6]}]
set_property PACKAGEPIN V14 [get_ports {led[7]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[7]}]
set_property PACKAGEPIN V13 [get_ports {led[8]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[8]}]
set_property PACKAGEPIN V3 [get_ports {led[9]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[9]}]
set_property PACKAGEPIN W3 [get_ports {led[10]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[10]}]
set_property PACKAGEPIN U3 [get_ports {led[11]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[11]}]
set_property PACKAGEPIN P3 [get_ports {led[12]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[12]}]
set_property PACKAGEPIN N3 [get_ports {led[13]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[13]}]
set_property PACKAGEPIN P1 [get_ports {led[14]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[14]}]
set_property PACKAGEPIN L1 [get_ports {led[15]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {led[15]}]
```

#7 segment display

```
set_property PACKAGEPIN W7 [get_ports {seg[0]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {seg[0]}]
set_property PACKAGEPIN W6 [get_ports {seg[1]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {seg[1]}]
set_property PACKAGEPIN U8 [get_ports {seg[2]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {seg[2]}]
set_property PACKAGEPIN V8 [get_ports {seg[3]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {seg[3]}]
set_property PACKAGEPIN U5 [get_ports {seg[4]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {seg[4]}]
set_property PACKAGEPIN V5 [get_ports {seg[5]}]
        set_property IOSTANDARD LVCMOS33 [get_ports {seg[5]}]
set_property PACKAGEPIN U7 [get_ports {seg[6]}]
```




```
set_property IOSTANDARD LVCMOS33 [get_ports {seg[6]}]

set_property PACKAGE_PIN U2 [get_ports {an[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {an[0]}]
set_property PACKAGE_PIN U4 [get_ports {an[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {an[1]}]
set_property PACKAGE_PIN V4 [get_ports {an[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {an[2]}]
set_property PACKAGE_PIN W4 [get_ports {an[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {an[3]}]

##Buttons
set_property PACKAGE_PIN U18 [get_ports rst]
    set_property IOSTANDARD LVCMOS33 [get_ports rst]
```



Chapter 4

Testing and Results

4.1 Simulation Results

The individual modules were simulated using Vivado. The following results were observed:

- Clock divider outputs verified for 1 Hz and slower clock frequencies.
- Game logic accurately tracked scores and timer functionality.
- Binary to BCD conversion correctly translated binary values for display.
- Multiplexer and decoder outputs successfully controlled the seven-segment displays.

4.2 Hardware Testing

The design was implemented on the Basys 3 FPGA board, and the following were observed:

- Real-time updates on the seven-segment displays for timer and score.
- LED transitions simulated mole behavior effectively.
- Switch inputs registered user actions accurately.



Chapter 5

Conclusion and Future Work

5.1 Conclusion

The Whack-a-Mole game was successfully implemented on the Basys 3 FPGA board. It demonstrated the effective use of hardware resources for real-time applications and provided an engaging way to interact with FPGA hardware.

5.2 Future Enhancements

- Add more complex game logic to increase difficulty levels.
- Implement sound feedback for user interactions.
- Explore power optimization techniques for the design.